

```
In[57]:= R1 := 3.3
         R2 := 985
         R3 := 901
         sigmaR3 := 11.000
         sigmaR2 := 11.000
         sigmaR1 := 3.3 * 0.05
```

```
In[63]:= sigmaR1
```

```
Out[63]= 0.165
```

```
In[64]:= U := 2.01
         sigmaU := 0.022
```

```
In[66]:= Rg = 1 / (1 / R1 + 1 / R3)
```

```
Out[66]= 3.28796
```

```
In[67]:= sigmaRg =  $\left(\frac{1}{R1} + \frac{1}{R3}\right)^{-2} \sqrt{\left(\frac{\text{sigmaR1}}{R1^2}\right)^2 + \left(\frac{\text{sigmaR3}}{R3^2}\right)^2}$ 
```

```
Out[67]= 0.163798
```

```
In[68]:= Ig =  $\frac{U}{Rg + R2}$ 
```

```
Out[68]= 0.00203382
```

```
In[69]:= sigmaIg =  $\sqrt{\left(\frac{\text{sigmaR2 } U}{(R2 + Rg)^2}\right)^2 + \left(\frac{\text{sigmaRg } U}{(R2 + Rg)^2}\right)^2 + \left(\frac{\text{sigmaU}}{R2 + Rg}\right)^2}$ 
```

```
Out[69]= 0.0000317505
```

Integratorstrom

```
In[70]:= Iint =  $\frac{Ig}{\left(\frac{R3}{R1} + 1\right)}$ 
```

```
Out[70]=  $7.42188 \times 10^{-6}$ 
```

```
In[71]:=
```

```
In[72]:= sigmaIint =  $\sqrt{\left(\frac{Ig R3 \text{ sigmaR1}}{R1^2 \left(\frac{R3}{R1} + 1\right)^2}\right)^2 + \left(\frac{Ig \text{ sigmaR3}}{R1 \left(\frac{R3}{R1} + 1\right)^2}\right)^2 + \left(\frac{\text{sigmaIg}}{\frac{R3}{R1} + 1}\right)^2}$ 
```

```
Out[72]=  $3.97848 \times 10^{-7}$ 
```